 


# Block diagram of ROM chip



# To construct a 2 KB RAM chip

## How many 128 B RAM chips are required?

Big RAM chip size = 2 KB =  $2^1 \times 2^{10}$  B =  $2^{11}$  B

Available small RAM chip size = 128 B =  $2^7$  B

Number of 128 B RAM chips require =

$$\begin{aligned} &= \frac{\text{Big RAM chip size}}{\text{Available small RAM chip size}} \\ &= \frac{2^{11} \text{ B}}{2^7} \\ &= 2^4 \text{ B} \\ &= 16 \end{aligned}$$

# Design a big RAM chip using small RAM chips

To construct a 256 B RAM chip How many 128 B RAM chips are required?

Big RAM chip size = 256 B

Available small RAM chip size = 128 B

Number of 128 B RAM chips =


$$\begin{aligned} &= \frac{\text{Big RAM chip size}}{\text{Available small RAM chip size}} \\ &= \frac{256 \text{ B}}{128 \text{ B}} \\ &= 2 \end{aligned}$$

Number of Address bits for small RAM chip = 7 ( $A_6 - A_0$ )


Number of Address bits for big RAM chip = 8 ( $A_7 - A_0$ ) [Click here](#)

Number of Data bits for big RAM chip and small RAM chip are same and is equal to 8 ( $D_7 - D_0$ )


# Memory connection to the CPU

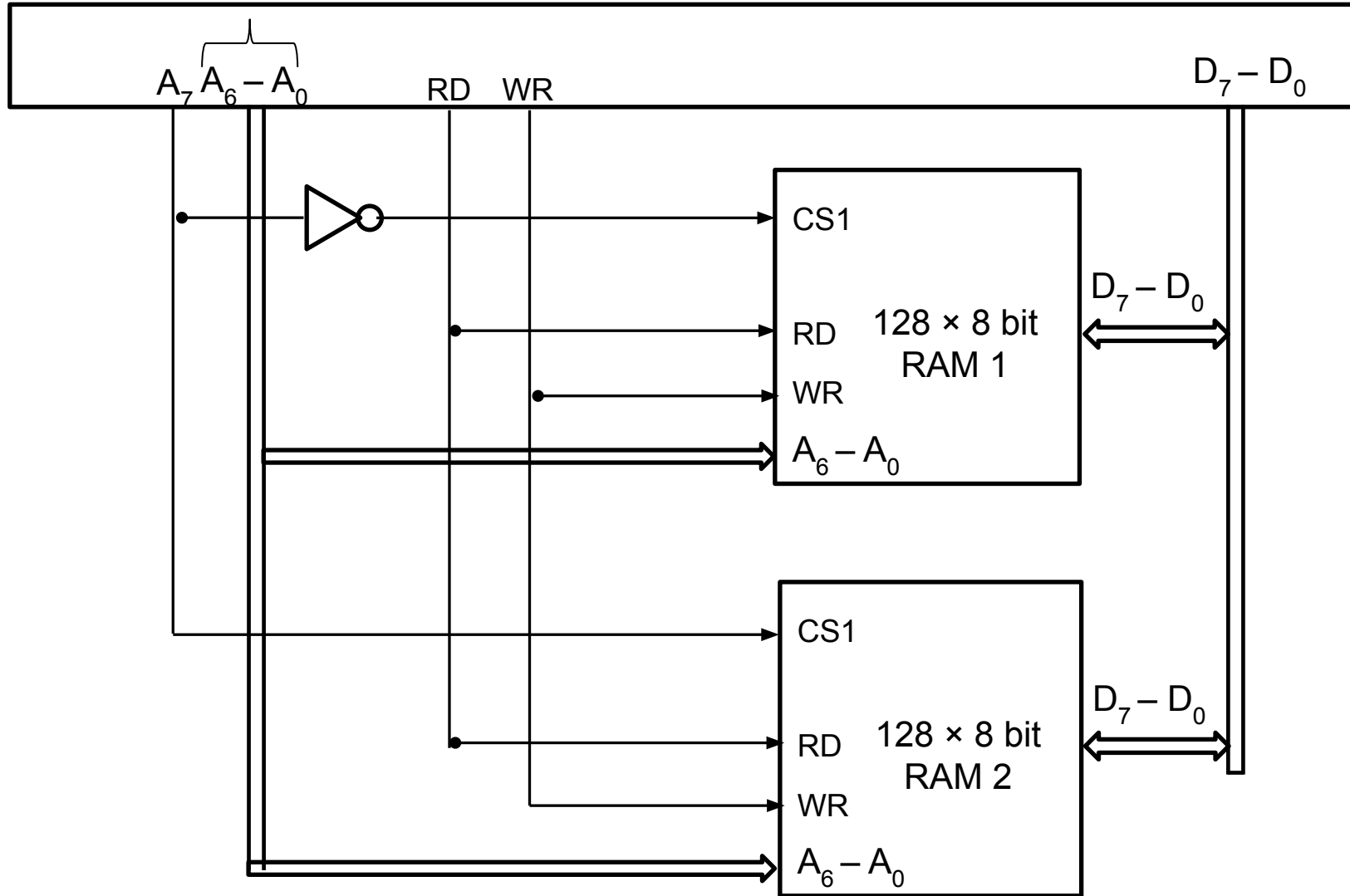

# Memory Read operation from RAM 1

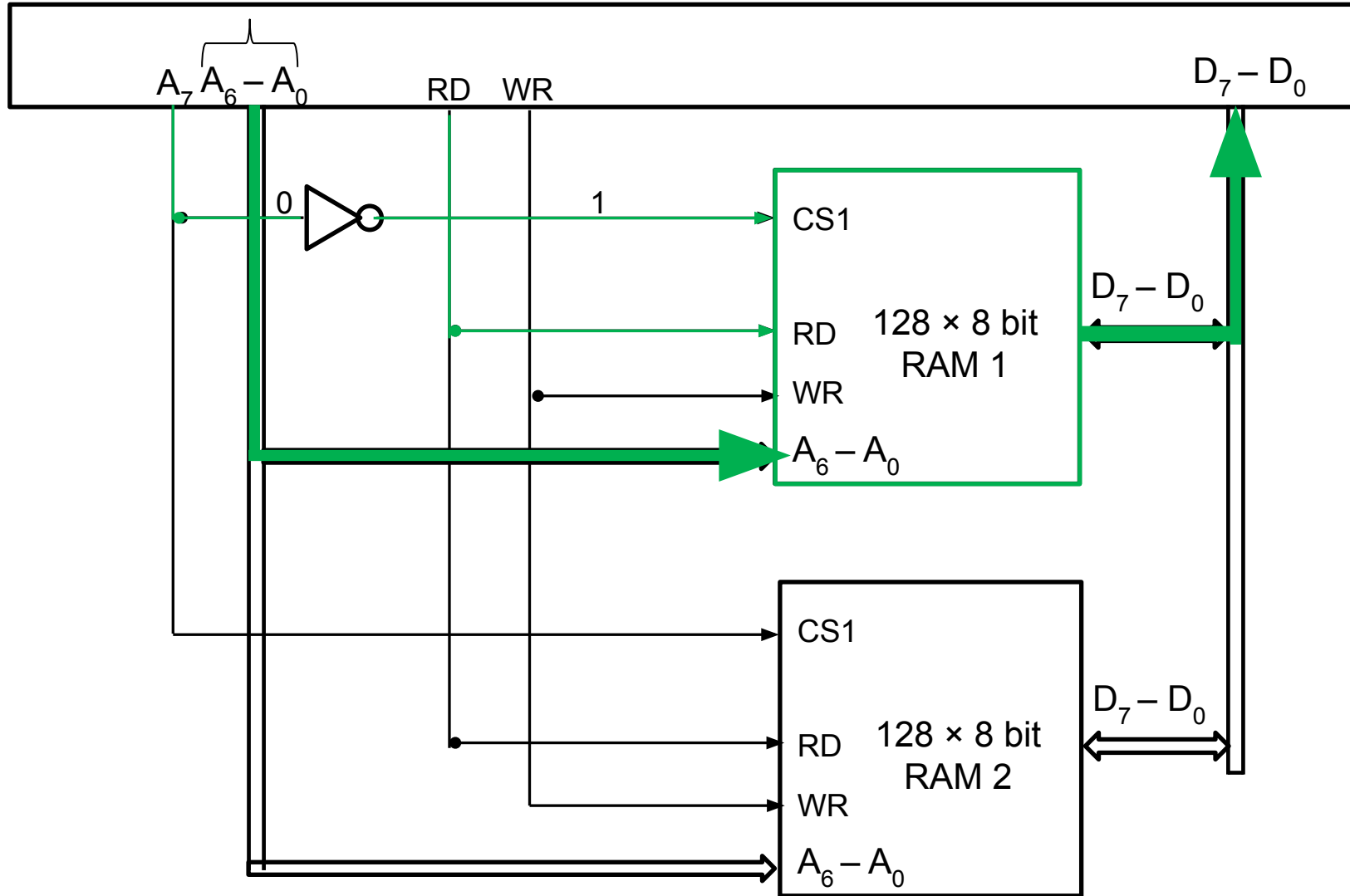

# Memory Write operation into RAM 2

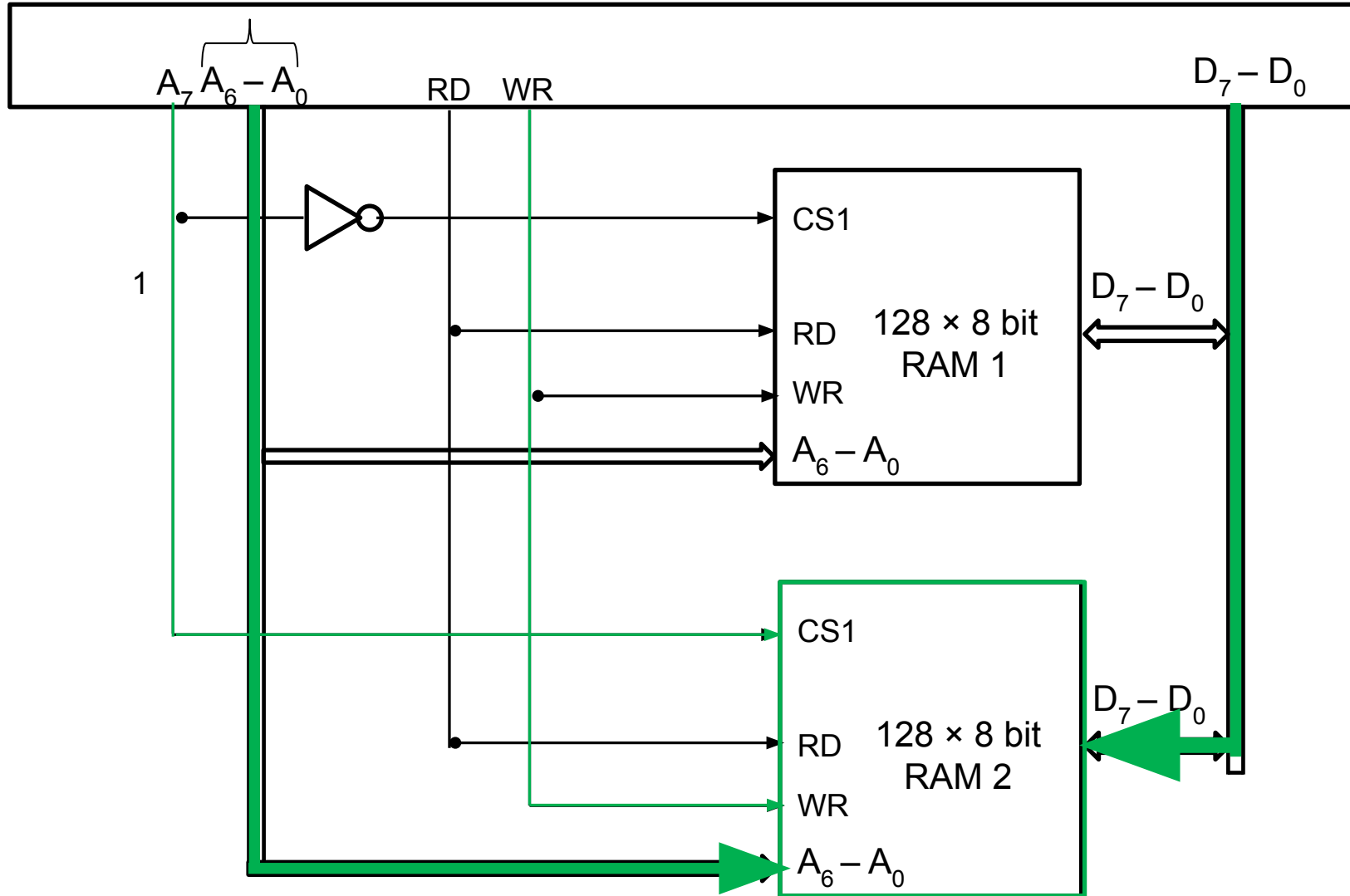

# Memory Address Map

Component	Hexadecimal Address	Address bus							
		A <sub>7</sub>	A <sub>6</sub>	A <sub>5</sub>	A <sub>4</sub>	A <sub>3</sub>	A <sub>2</sub>	A <sub>1</sub>	A <sub>0</sub>
RAM 1	00 – 7F	0	×	×	×	×	×	×	×
RAM 2	80 – FF	1	×	×	×	×	×	×	×

[Click here](#)

# Design a big RAM chip using small RAM chips

## contd.

To construct a 1 KB RAM chip How many 256 B RAM chips are required?

Big RAM chip size = 1 KB = 1024 B

Available small RAM chip size = 256 B

Number of 256 B RAM chips require =

$$\begin{aligned} &= \frac{\text{Big RAM chip size}}{\text{Available small RAM chip size}} \\ &= \frac{1024 \text{ B}}{256 \text{ B}} \\ &= 4 \end{aligned}$$

Number of Address bits for small RAM chip = 8 ( $A_7 - A_0$ )

Number of Address bits for big RAM chip = 10 ( $A_9 - A_0$ )

Number of Data bits for big RAM chip and small RAM chip are same and is equal to 8 ( $D_7 - D_0$ )




# Memory Address Map

Component	Hexadecimal Address	Address bus									
		A <sub>9</sub>	A <sub>8</sub>	A <sub>7</sub>	A <sub>6</sub>	A <sub>5</sub>	A <sub>4</sub>	A <sub>3</sub>	A <sub>2</sub>	A <sub>1</sub>	A <sub>0</sub>
RAM 1	0000 – 00FF	0	0	×	×	×	×	×	×	×	×
RAM 2	0100 – 01FF	0	1	×	×	×	×	×	×	×	×
RAM 3	0200 – 02FF	1	0	×	×	×	×	×	×	×	×
RAM 4	0300 – 03FF	1	1	×	×	×	×	×	×	×	×


[Click here](#)

# Memory connection

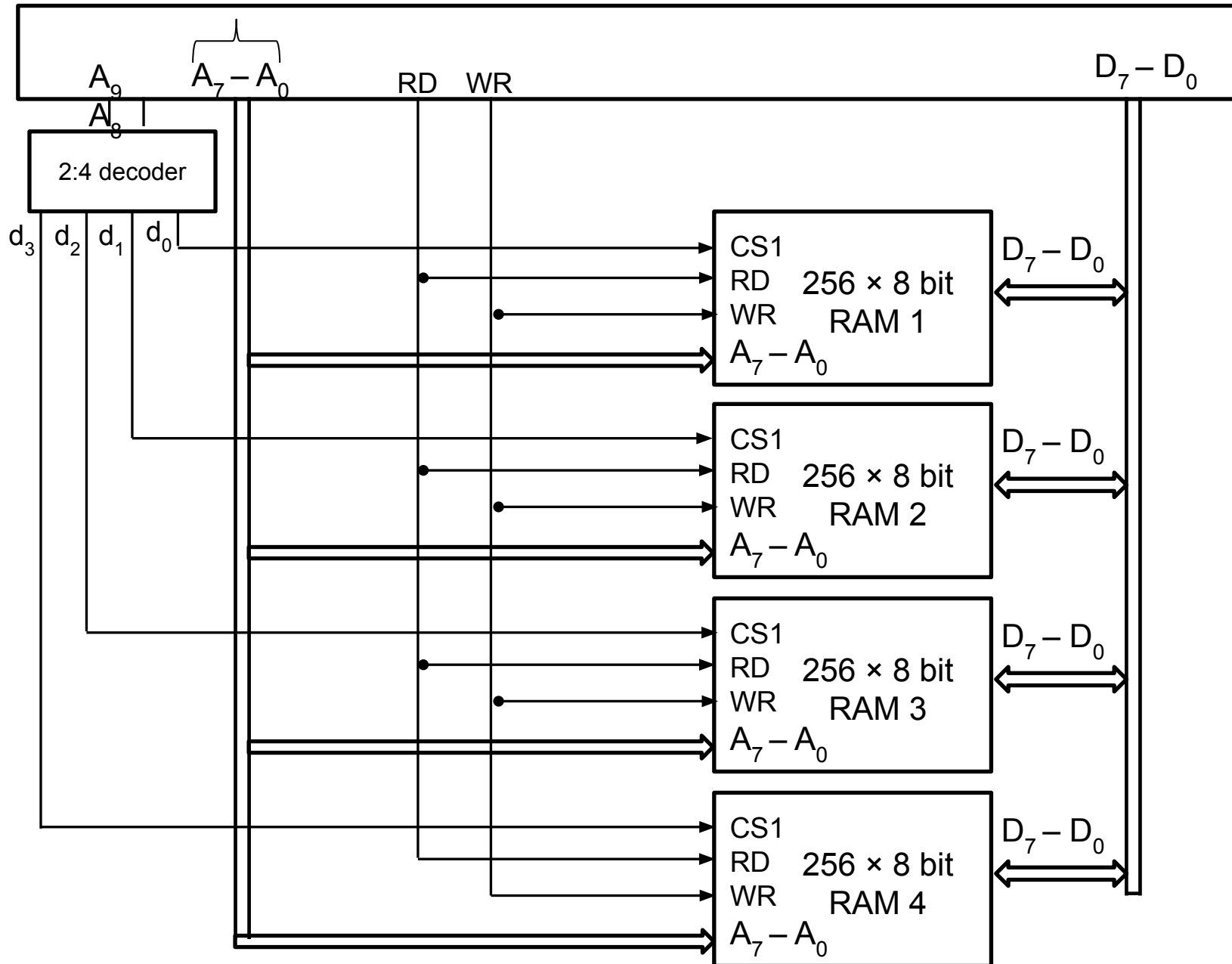


[Click here](#)

Thank You

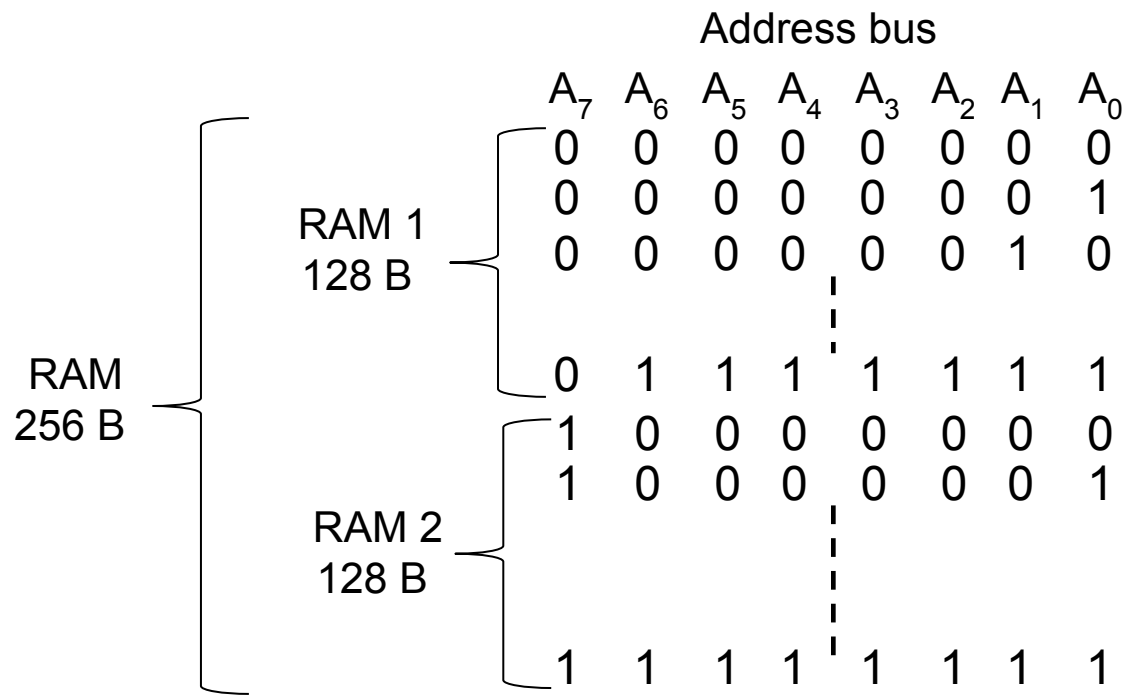

Back

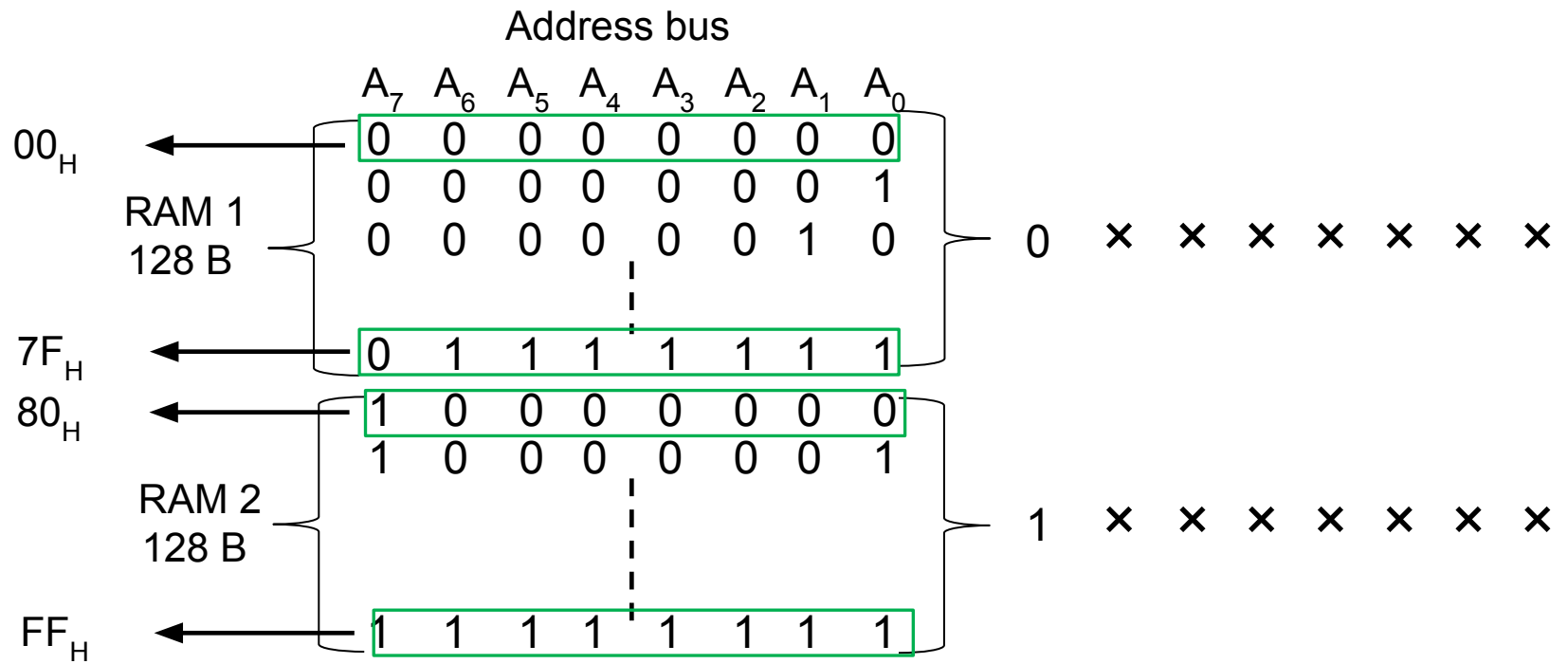

Back



# Decoder Specification


$N : 2^N$  Decoder  $\Rightarrow$   $N$  inputs and  $2^N$  outputs

2 : 4 Decoder  $\Rightarrow$  2 inputs and 4 outputs

3 : 8 Decoder  $\Rightarrow$  3 inputs and 8 outputs

4 : 16 Decoder  $\Rightarrow$  4 inputs and 16 outputs

# Decoder

 

Back