

# Design a big memory chip using small RAM and ROM chips

To construct a 512 B RAM chip four 128 B RAM chips are required.

$$\begin{array}{c} \overline{1024} \\ 1024 \\ 2 \end{array} \quad \begin{array}{c} 10 \\ 2 \end{array}$$

$A_9 - A_0$

Number of Address bits for small RAM chip = 7 ( $A_6 - A_0$ )


Number of Address bits for ROM chip = 9 ( $A_8 - A_0$ )

# Memory Address Map

Component	Hexadecimal Address	Address bus									
		A <sub>9</sub>	A <sub>8</sub>	A <sub>7</sub>	A <sub>6</sub>	A <sub>5</sub>	A <sub>4</sub>	A <sub>3</sub>	A <sub>2</sub>	A <sub>1</sub>	A <sub>0</sub>
RAM 1	0000 – 007F	0	0	0	×	×	×	×	×	×	×
RAM 2	0080 – 00FF	0	0	1	×	×	×	×	×	×	×
RAM 3	0100 – 017F	0	1	0	×	×	×	×	×	×	×
RAM 4	0180 – 01FF	0	1	1	×	×	×	×	×	×	×
ROM	0200 – 03FF	1	×	×	×	×	×	×	×	×	×

[Click here](#)

[Back](#)

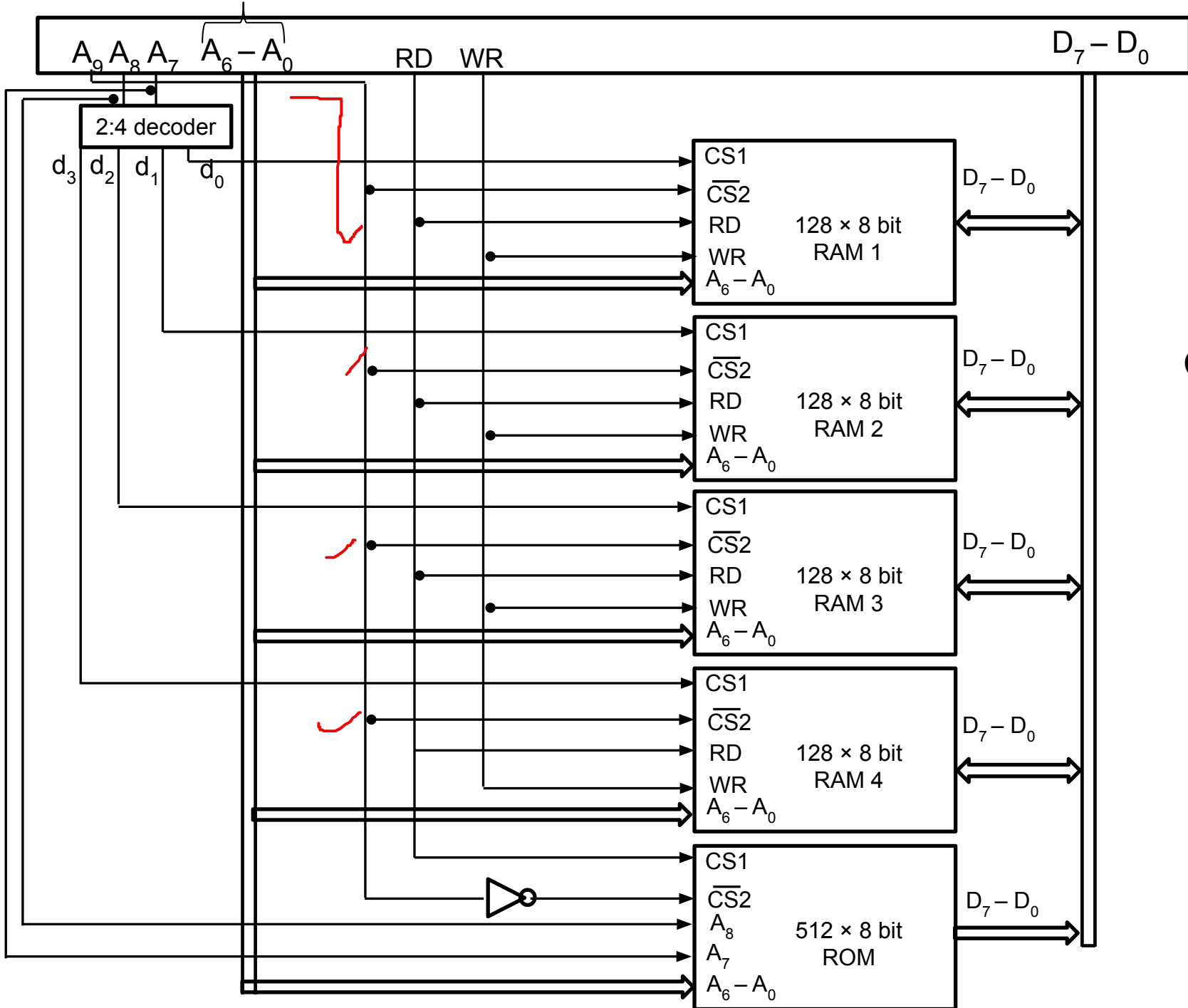

Click here

# Design a big RAM chip using small RAM chips where data bits are different

To construct a 64 K × 16 bit RAM chip How many 16KB RAM chips are required?

Big RAM chip size = 64 K × 16 bit

Available small RAM chip size = 16 K × 8 bit

Number of 16 KB RAM chips require =

$$\frac{\text{Big RAM chip size}}{\text{Available small RAM chip size}}$$

$$\frac{64 \text{ K} \times 16}{16 \text{ K} \times 8}$$

$$= 4 \times 2 = 8$$


Number of Address bits for small RAM chip = 14 ( $A_{13} - A_0$ )

Number of Address bits for big RAM chip = 16 ( $A_{15} - A_0$ )


Number of Data bits for small RAM chip = 8 ( $D_7 - D_0$ )

Number of Data bits for big RAM chip = 16 ( $D_{15} - D_0$ )

# Memory connection

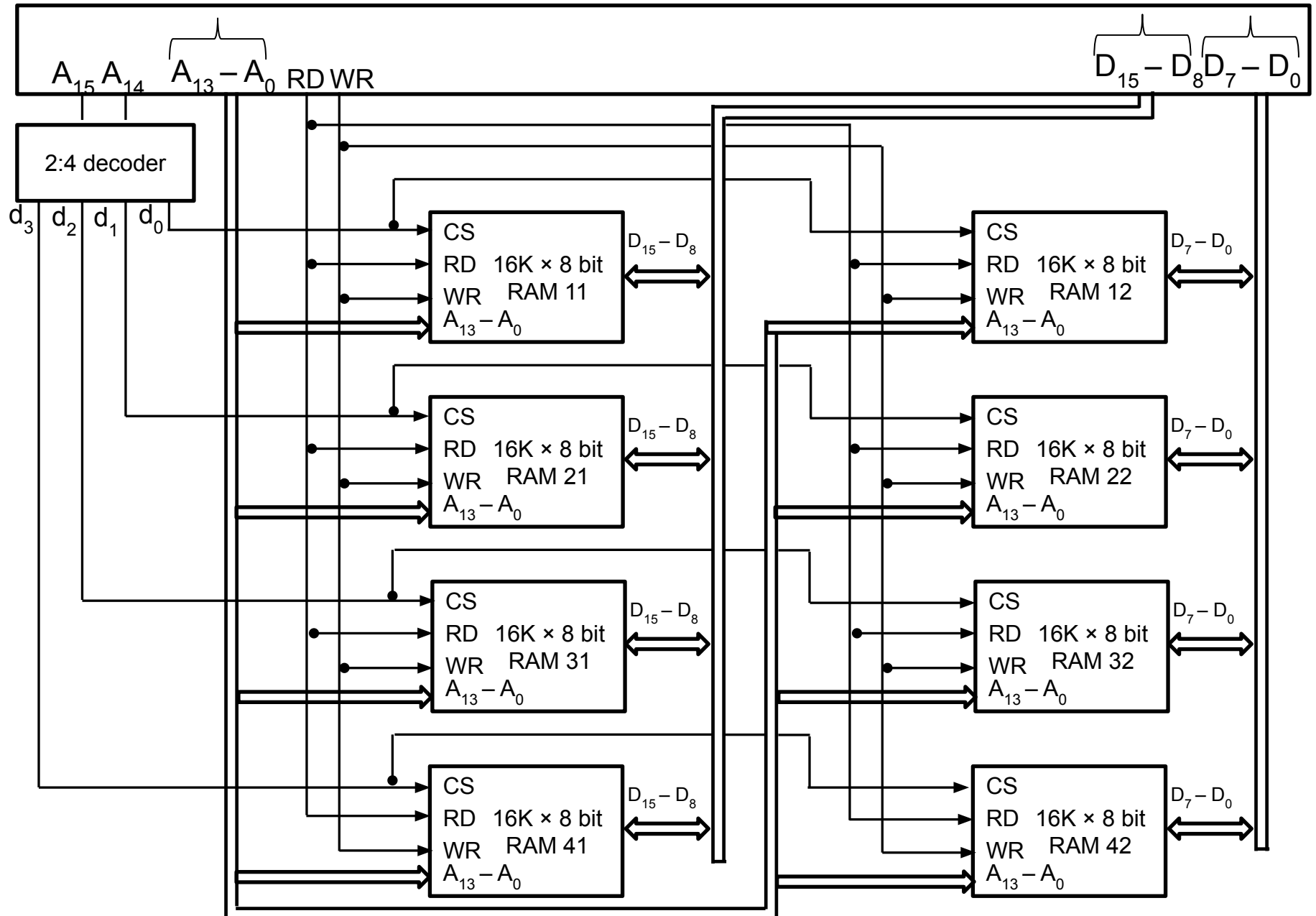

Thank You

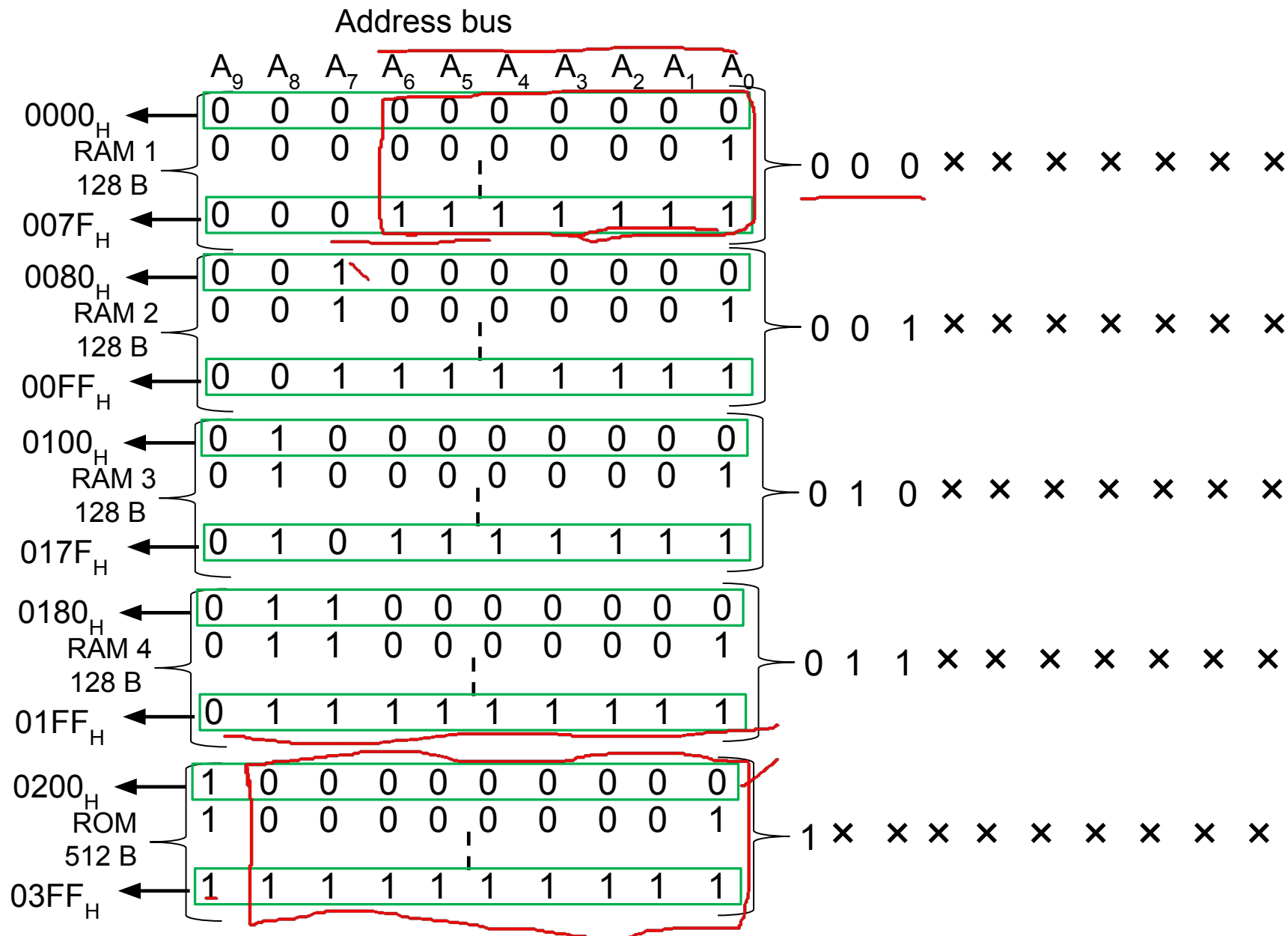

Back